

Arquiteturas de Alto Desempenho 2024/2025

Second practical assignment — VHDL description and simulation of an indexed accumulator

Tomás Oliveira e Silva

1 Work to be done

The main purpose of this assignment is to write a VHDL description of a sequential logic circuit that implements the following C function:

```
unsigned int acc(unsigned int w_addr,unsigned int inc,unsigned int r_addr)
{
    static unsigned int a[16]:
    unsigned int r;

    r = a[r_addr % 16];
    a[w_addr % 16] += inc;
    return r;
}
```

The implementation has to receive one value of each of its arguments in each clock cycle. Use the following entity declaration:

```
entity accumulator is
    generic
    (
        ADDR_BITS : integer range 2 to 8 := 4;
        DATA_BITS : integer range 4 to 32 := 8
    );
    port
    (
        clock      : in std_logic;
        -- write port
        write_addr  : in  std_logic_vector(ADDR_BITS-1 downto 0);
        write_inc   : in  std_logic_vector(DATA_BITS-1 downto 0);
        -- read port
        read_addr   : in  std_logic_vector(ADDR_BITS-1 downto 0);
        read_data   : out std_logic_vector(DATA_BITS-1 downto 0)
    );
end accumulator;
```

A write enable signal is not needed: when no accumulation is desired just use any write address and a zero increment. This simplifies the implementation.

The work has four parts. For each of them provide an architecture and a testbench.

1. **[Mandatory]** Single-cycle implementation: do the read, addition and write operations in the same clock cycle.
2. **[Highly recommended]** Multi-cycle implementation: do the read, addition and write operations in three clock cycles (one for each). Be aware: you must deal with the situation when the same write address is used in consecutive clock cycles.
3. **[Optional]** Do at least one of the two previous items for the following modified accumulator.

```
unsigned int acc(unsigned int w_addr,unsigned int inc,unsigned int shift,unsigned int r_addr)
{
```

```

static unsigned int a[16]:
unsigned int r;

r = a[r_addr % 16];
a[w_addr % 16] += inc << (shift % 32);
return r;
}


```

For that you must implement an efficient barrel-shifter entity. (Just create an entity that shifts or not an input vector by a fixed number of bits, and instantiate it several times in tandem for shifts of 1, 2, 4, etc., and use appropriate control signals.)

In your accumulator use the adder_n entity of the P10 class. Also, modify and use the dual_port_ram entity of the P11 class.

2 Possible block diagram for the first work item

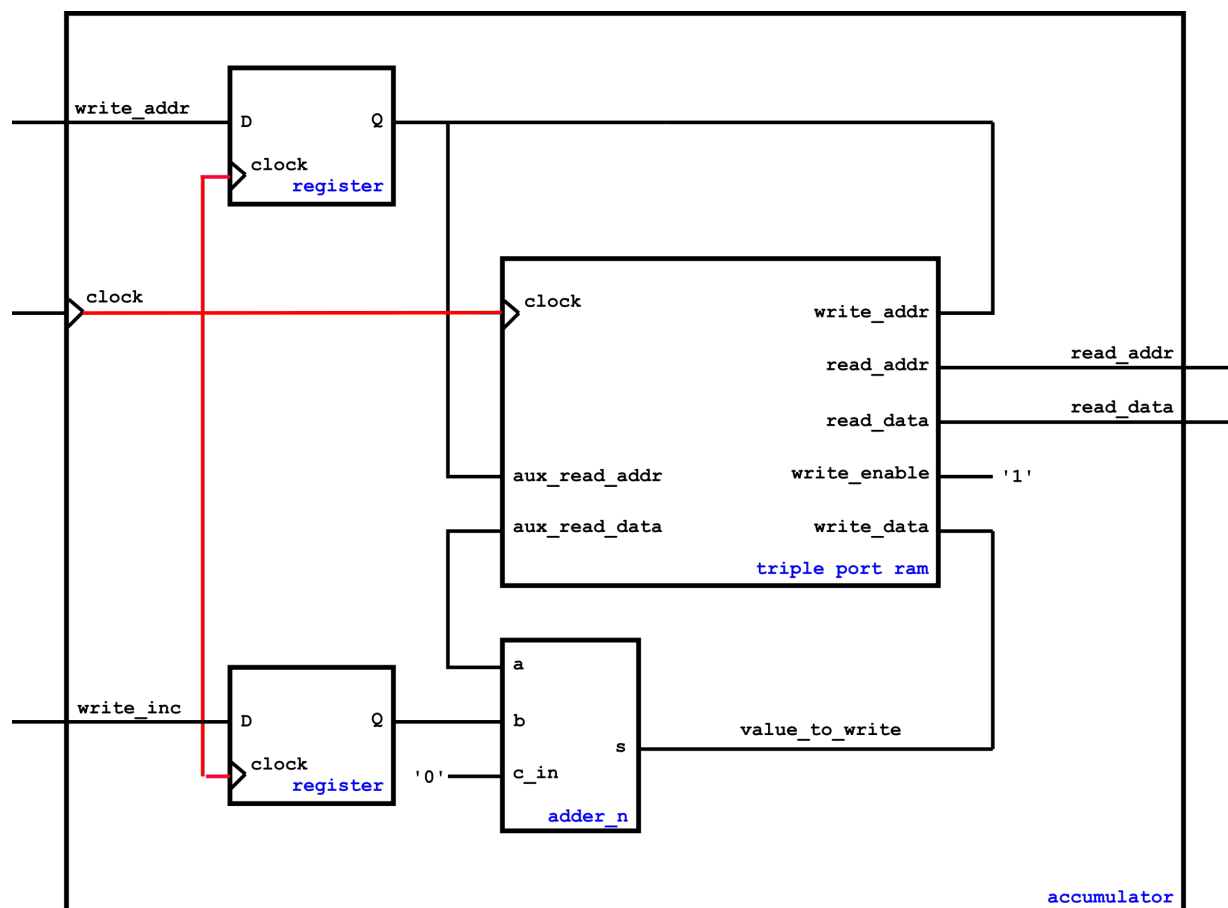The following figure presents a possible implementation of the first part of the work. The aux read port is synchronous or asynchronous?



To do part 3 in single-cycle mode, place the barrel shifter either between write_inc and b or between s and write_data.